



Zeno Martini (admin)



RESISTENZA PURA

1 January 2004

$$u(t) = U_M \cdot \sin \omega t$$

$$i(t) = I_M \cdot \sin \omega t$$
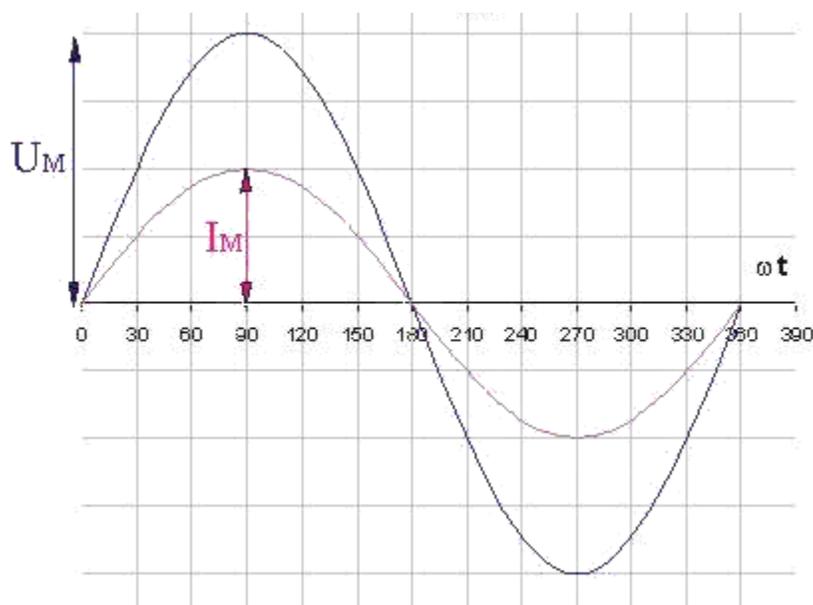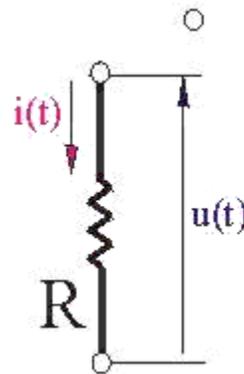
$$I_M = \frac{U_M}{R} \quad \omega = 2\pi f$$



$$\dot{U} = \frac{U_M}{\sqrt{2}} \angle 0$$

$$\dot{i} = \frac{I_M}{\sqrt{2}} \angle 0$$

$$\dot{U} = R \cdot \dot{i}$$

